

QZ-EE-001 Circuits Quiz

Give all answers as numbers without units attached.


Your email address (rpetitti@tollestechn.com) will be recorded when you submit this form. Not **rpetitti**?

[Sign out](#)

* Required

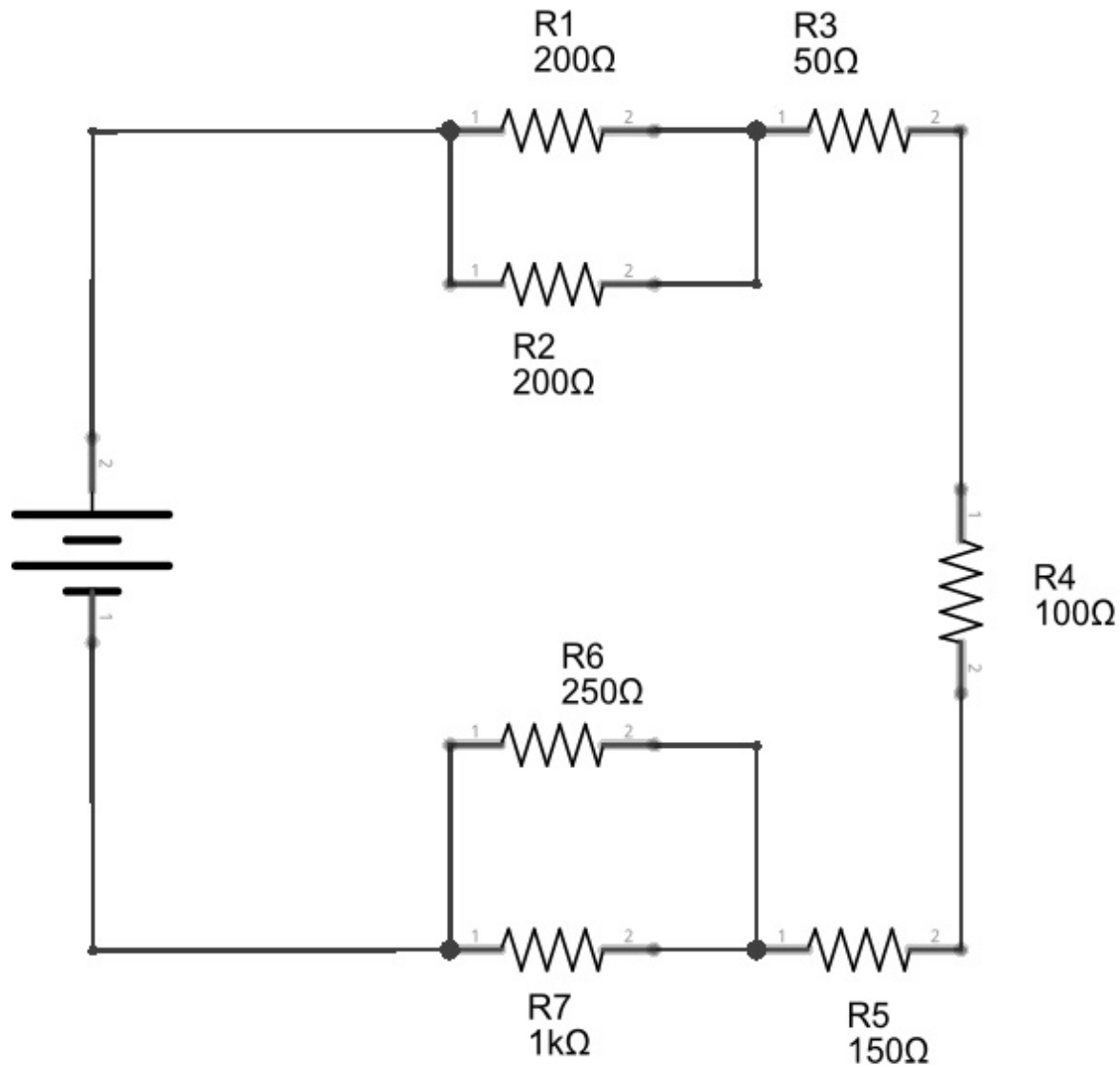1. Name *

Given a 100V battery, and assuming ground is the bottom of the circuit:



2. What is the equivalent resistance? (Round to the nearest whole ohm)

3. What is the current running through the circuit? (Round to the nearest .01)

4. What is the power generated by the circuit? (Round to the nearest .01)

☐ Send me a copy of my responses.

Powered by
 Google Forms